COMPUTER SYSTEMS AND ORGANIZATION Part 1

Daniel Graham



REVIEW





push to close

push to open









Y

Source of Voltage (VDD)





NAND



$Y = \overline{AB}$



Circuit with a NAND Gate







We don't normally draw the voltage and ground with gates. So, you will normally see circuits that look like this.



CHIPS WITH NAND GATES



























A	B	С	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

WHAT IS THE OUTPUT OF THIS CIRCUIT?





EXPRESS CIRCUIT AS AN EQUATION



Write the equation representing the circuit. Note: I replaced the OR with a NOR. What's missing from the equation below:

(A and B) or ((B and C) & (B or C))

EXAM QUESTION



7. (2 points) Consider the following-push-pull network. Which gate does it implement? (Hint: write out the truth table.)
Pull up pull down



Pull up pull down

Figure 1: Push-Pull-Network, output is the unlabeled wire on the right.

⊖ AND

 \bigcirc OR

O NAND

○ XOR

○ NOR

 \bigcirc None of the above

CREATIVE QUESTIONS



NAND GATES ARE TURNING COMPLETE

It is possible to implement every other gate by using a NAND. You can implement the complete RISC-V architecture using only NAND gates. What a beautiful building block right ⁽²⁾

Use a NAND gate to implement the following gates:

- 1. NOT
- 2. AND
- 3. OR
- 4. NOR
- 5. XOR

Hint: Start by asking NOT what a NAND gate can do for you but what you can do with a NAND gate.





TODAY'S LECTURE





- 1. Towards building a digital adding machine
- 2. How can we represent numbers? (What about decimals and negative numbers)

GREAT WE HAVE GATES NOW LET'S BUILD SOMETHING. HOW ABOUT A MACHINE THAT ADDS NUMBERS?



THE IDEA





THE CHALLENGE

Our gates only support 0 and 1s.

How can we represent other decimal numbers?

How can we present negative numbers?

What about fractions \odot ?

DECIMAL

- Decimal numbers
 - 1's column 10's column 100's column 1000's column
 - $5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$

 five	three	seven	four
thousands	hundreds	tens	ones



BINARY





BINARY CONVERSION EXAMPLES

Convert 74 to binary = 1001010

74 ÷ 2 = 37	remainder 0
37 ÷ 2 = 18	remainder 1
18 ÷ 2 = 9	remainder 0
9 ÷ 2 = 4	remainder 1
4 ÷ 2 = 2	remainder 0
2 ÷ 2 = 1	remainder 0
1 ÷ 2 = 0	remainder 1

Convert 10101 to Decimal



EXAM REVIEW

1 Binary and Hex

1. (2 points) Convert 45_{10} (base 10) to binary. the box so that the grader can see it.)



 (2 points) Write 132₁₀ in base 5. Use the space below for rough work, but remember to write your final answer in the box.





 (2 points) Write 132₁₀ in base 5. Use the space below for rough work, but remember to write your final answer in the box.



EXAM QUESTION SIMPLIFIED



NOW LET'S BUILD A MACHINE WITH GATES THAT WILL ADD



4-BIT ADDER







INPUTS AND OUTPUT OF OUR ADDER

What would the input be if we wanted to add 5, and 9?

Notice we need to pick and order for the wires.

Which output lights would we want to light up?

A

В



INPUTS AND OUTPUT OF OUR ADDER

Α

В

What if we now added 7 and 9? What would our inputs be, and which lights do we expect to light up?



LET'S DESIGN THE CIRCUIT THAT WILL IMPLEMENT THIS ADDER



LET'S START A MACHINE THAT ADDS TWO BITS

Draw Half Adder



Let's start by building a half adder something that just adds two bits.

Let's build a truth table.

А	В	A + B	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

LET'S START SIMPLE (MACHINE THAT ADDS TWO BITS)



HALF ADDER

Let's start by building a half adder something that just adds two bits.

Let's build a truth table.

А	В	A + B	C.out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

We can implement A + B with an XOR gate And the C.out (Carry out) With an AND gate





HALF ADDER DEMO



https://tinyurl.com/ygpea8v4

http://www.falstad.com/circuit/circuitjs.html?ctz= CQAgjCAMB0l3BWc0FwCwCY0HYEA4cEMElURTJy BTAWjDACgwE0QMs21KBmANj06VKGKOSZl2rMGl Z8B01sNEIGAGXAZ5vSnkphtbUQDMAhgBsAzlXJQ 1GgZJC62HEZVOXrSSAwDu9lykDRx9fWEOclDQ8AMwTUDov1il1kcQ5PitPQBOESiYsDyU 8GLiXlswsoQK9JrK0vzgylMfAFkQOXAZEDR9brS2F AYOrqxKPtquQwxhoA



